

Exam I

E210/B441, Spring 2021

Name: _____ **KEY** _____

Email: _____

I have neither **given** nor **received** unauthorized aid on this examination, nor have I **concealed** any knowledge of unauthorized aid by others.

Signature: _____

Name: _____

Email: _____


This page intentionally left blank.

Name: _____

Email: _____

 1. Boolean Logic Part 1 (10 Points) (Released Early)

Construct the truth table for the following circuit:



Inputs			Outputs			
A	B	C	D	E	F	G
0	0	0	0	1	0	1
0	0	1	0	0	1	1
0	1	0	0	0	0	1
0	1	1	0	1	1	1
1	0	0	0	1	0	1
1	0	1	0	0	1	1
1	1	0	1	1	1	1
1	1	1	1	0	0	0

Name: _____

Email: _____

2. Boolean Logic Part 2 (10 Points)

Write the SystemVerilog module definition that implements the following truth table below. A, B, and C are inputs. X and Y are outputs. Note, this does **NOT** have to utilize *minimized* Boolean logic.

<u>Inputs</u>			<u>Outputs</u>	
A	B	C	X	Y
0	0	0	1	0
0	0	1	0	0
0	1	0	0	1
0	1	1	1	1
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

(5 pts per assign, 1 pts per equation, 1 pt for correct OR)

```
module truth_table (
    input a, b, c,
    output x, y
);
```

X and Y are reversed for some

```
assign x = (~a & ~b & ~c) | (~a & b & c) |
           ( a & ~b & ~c) | ( a & b & c);
```

```
assign y = (~a & b & ~c) | (~a & b & c) |
           ( a & ~b & ~c) | ( a & ~b & c);
```

-- OR --

```
assign x = ~ (b ^ c);
assign y =  (a ^ b);
```

```
endmodule
```

3. Multiplexer & Testbench (20 points)

- a. (6 pts) A Multiplexer (or Mux) is a device that selects between several digital inputs and forwards the selected input to a single output line. The selection is directed by a separate set of inputs known as select lines. A multiplexer of 2^n inputs has n select lines, which are used to select which input line to send to the output. [wiki]

Please implement a 2-input multiplexer in SystemVerilog below. If $s==0$, the output z should match the input a , otherwise z should match input b .

```
module mux2 (  
    input      a,  
    input      b,  
    input      s,  
    output logic z  
);  
  
    always_comb begin  
        z = a; //default  
        if (s == `h1)  
            z = b;  
    end  
  
    -- OR --  
  
    assign z = (s == `h0 ? a : b);  
  
    -- OR --  
  
    assign z = (a & ~s) | (b & s);  
  
endmodule
```

Name: _____

Email: _____

- b. (12 pts) Please implement a testbench for the 2-input multiplexer in SystemVerilog. To receive all points, your testbench should test all possible inputs. **BUGFIX**

1 pt for each test case (8x), 1 pt for setting a,b,s, 1 pt for assert, 1pt delay, 1 pt for \$display/\$finish

```
module mux2_tb();

    logic a,b;
    logic s;
    wire  z;

    mux2 DUT (.a(a), .b(b), .s(s), .z(z) );

    task mux2Test(
        input aT, bT, sT, zT
    );

        a = aT; b = bT; s = sT;
        #1
        assert( z == zT ) else
            $fatal(1, "bad:  a:%b b:%b s:%b z:%b, zT:%b", a, b, s,
z, zT);
    endtask

    initial begin

        mux2Test(0,0,0,0); //1'h0 or `h0 also work
        mux2Test(0,0,1,0);
        mux2Test(0,1,0,0);
        mux2Test(0,1,1,1);

        mux2Test(1,0,0,1);
        mux2Test(1,0,1,0);
        mux2Test(1,1,0,1);
        mux2Test(1,1,1,1);

        $display("@@@Passed");
        $finish();
    end

endmodule
```

4. More Multiplexer (10 points)

Please implement an 8-input multiplexer in SystemVerilog below. This time s should select the corresponding bit within the input in . **Your module must utilize mux2 from above.** You may assume a correct mux2 implementation.

1 pt /level 1 mux, 2 pts /level 2 mux

```

module mux8 (
    input    [7:0] in,
    input    [2:0] s,
    output   z
);


    wire [3:0] t; //temp - level 1
    wire [1:0] tt; //temp - level 2

    mux2 m0 (.a(in[0]), .b(in[1]), .s(s[0]), .z(t[0]) );
    mux2 m1 (.a(in[2]), .b(in[3]), .s(s[0]), .z(t[1]) );
    mux2 m2 (.a(in[4]), .b(in[5]), .s(s[0]), .z(t[2]) );
    mux2 m3 (.a(in[6]), .b(in[7]), .s(s[0]), .z(t[3]) );

    mux2 m4 (.a(t[0]), .b(t[1]), .s(s[1]), .z(tt[0]) );
    mux2 m5 (.a(t[2]), .b(t[3]), .s(s[1]), .z(tt[1]) );

    mux2 m6 (.a(tt[0]), .b(tt[1]), .s(s[2]), .z(z) );

```

 

```

endmodule


```

Name: _____

Email: _____

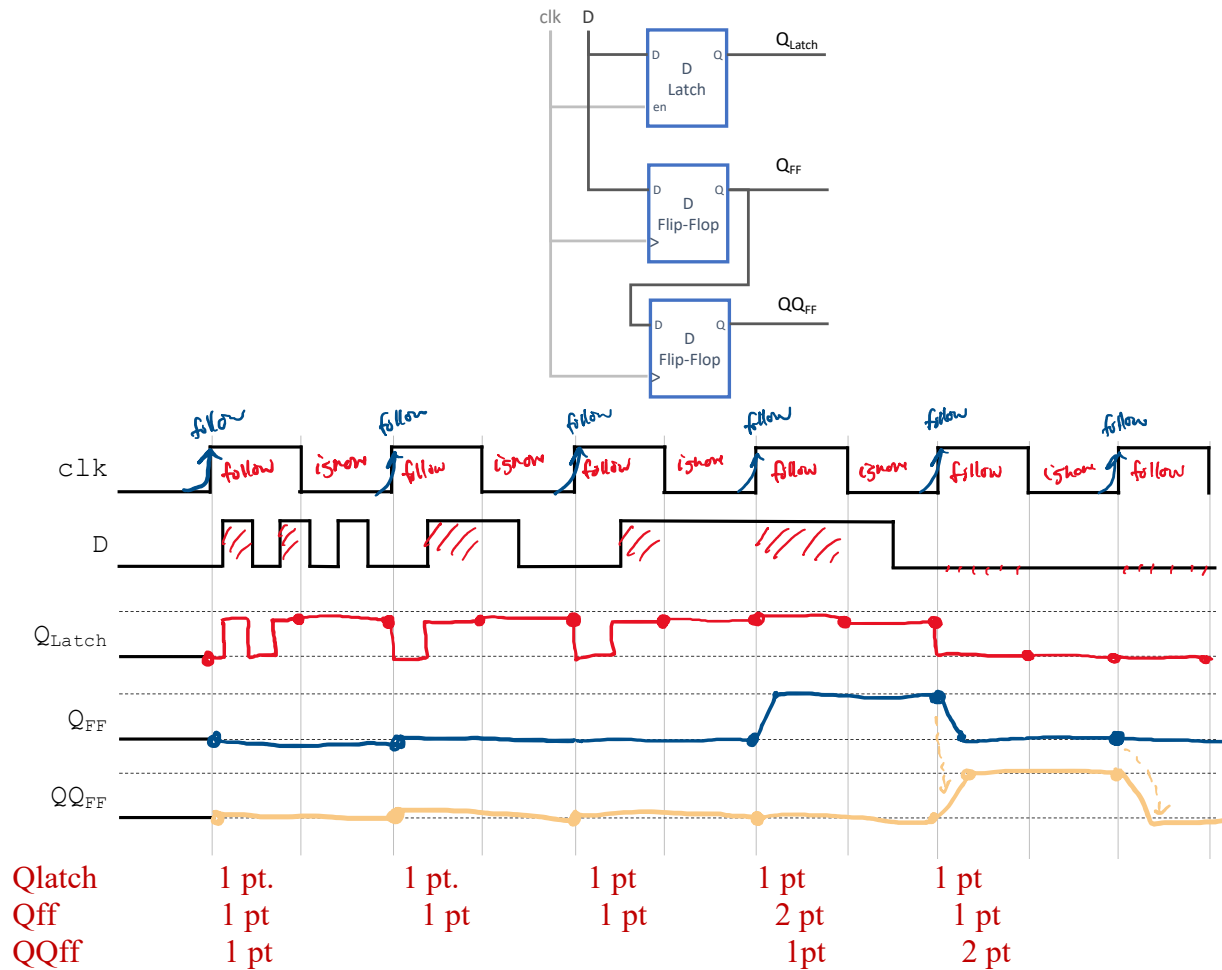5. Sequential Logic (15 Points)

Given the following circuit, draw the timing diagram of the outputs Q_{Latch} , Q_{FF} , and Q_{QFF} . You may assume all latches and flops initially output 0. Assume a small delay in the output of the latch or flip-flop.



6. State Machines (35 Points)


- a. (10 pts) A state table or a state transition diagram models the behavior of a clocked sequential circuit. **Draw a state transition diagram** for the state table shown below left. The table below right shows the output in each state. When reset is asserted ($rst == 1$) the state machine enters state $S0$. The input to the state machine is in , the output is out .

State	rst	in	Next state
X	1	X	$S0$
$S0$	0	1	$S0$
$S0$	0	0	$S1$
$S1$	0	0	$S1$
$S1$	0	1	$S2$
$S2$	0	0	$S2$
$S2$	0	1	$S0$

State	out
$S0$	0
$S1$	0/1
$S2$	1/0

Type 1
Type 2

1 pt per arrow, 1 pt per state

 

Name: _____

Email: _____

- b. **(25 pts) Write a SystemVerilog module** that implements the state machine described above. Assume that the frequency of the clock input *clk* does not need scaling. Code that results in inferred latches will be considered incorrect.

1pt enum states, 3 pt always_ff, 3pts output/state(9), 2pts/state transition(12)

```
module state_machine (
    input clk,
    input rst,
    input in,
    output logic out
);

enum {S0, S1, S2} state, nextState;

// Transition to next state
always_ff @(posedge clk) begin
    if ( rst )
        state <= S0;
    else
        state <= nextState;
end

// Next state + output function
always_comb begin
    nextState = state;
    case (state)
        S0: begin
            out = 1'b0;
            if (in) nextState = S1;
            else    nextState = S0; //optional
        end

        S1: begin
            out = 1'b0; // 1'b1
            if (in) nextState = S2;
            else    nextState = S1; //optional
        end

        S2: begin
            out = 1'b0; // 1'b0
            if (in) nextState = S0;
            else    nextState = S2; //optional
        end
    endcase
end

endmodule
```